

# **COMBINATIONAL LOGIC**


 


Fig. 4-1 Block Diagram of Combinational Circuit
 
## Binary addition by hand

- You can add two binary numbers one column at a time starting from the right, just like you add two decimal numbers.
- But remember it's binary. For example,  $1 + 1 = 10$  and you have to carry!





# HALF ADDER

## Adding two bits

- We'll make a hardware adder based on our human addition algorithm.
- We start with a **half adder**, which adds two bits X and Y and produces a two-bit result: a **sum** S (the right bit) and a **carry out** C (the left bit).
- Here are truth tables, equations, circuit and block symbol.

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0
  
$$\begin{aligned}C &= XY \\S &= X'Y + XY' \\&= X \oplus Y\end{aligned}$$



# FULL ADDER

## Adding three bits

- But what we really need to do is add *three* bits: the augend and addend bits, *and* the carry in from the right.
- A **full adder** circuit takes three inputs  $X$ ,  $Y$  and  $C_{in}$ , and produces a two-bit output consisting of a sum  $S$  and a carry out  $C_{out}$ .

$$\begin{array}{r} 1 \quad 1 \quad 1 \quad 0 \\ \quad 1 \quad 0 \quad 1 \quad 1 \\ + \quad 1 \quad 1 \quad 1 \quad 0 \\ \hline 1 \quad 1 \quad 0 \quad 0 \quad 1 \end{array}$$

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

## Full adder equations

- Using Boolean algebra, we can simplify  $S$  and  $C_{out}$  as shown here.

X	Y	$C_{in}$	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1



$$\begin{aligned}S &= \Sigma m(1,2,4,7) \\&= X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in} \\&= X'(Y'C_{in} + YC_{in}') + X(Y'C_{in}' + YC_{in}) \\&= X'(Y \oplus C_{in}) + X(Y \oplus C_{in})' \\&= X \oplus Y \oplus C_{in}\end{aligned}$$

$$\begin{aligned}C_{out} &= \Sigma m(3,5,6,7) \\&= X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in} \\&= (X'Y + XY')C_{in} + XY(C_{in}' + C_{in}) \\&= (X \oplus Y)C_{in} + XY\end{aligned}$$

  
# Full adder circuit

- We write the equations this way to highlight the hierarchical nature of adder circuits—you can build a full adder by combining two half adders!


$$S = X \oplus Y \oplus C_{in}$$
$$C_{out} = (X \oplus Y) C_{in} + XY$$



## A four-bit adder

 

 
- Similarly, we can cascade four full adders to build a four-bit adder.
  - The inputs are two four-bit numbers ( $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$ ) and a carry in  $CI$ .
  - The two outputs are a four-bit sum  $S_3S_2S_1S_0$  and the carry out  $CO$ .
- If you designed this adder without taking advantage of the hierarchical structure, you'd end up with a 512-row truth table with five outputs!




 
## An example of 4-bit addition


- Let's put our initial example into this circuit, with  $A=1011$  and  $B=1110$ .



1. Fill in all the inputs, including  $CI=0$
2. The circuit produces  $C1$  and  $S0$  ( $1 + 0 + 0 = 01$ )
3. Use  $C1$  to find  $C2$  and  $S1$  ( $1 + 1 + 0 = 10$ )
4. Use  $C2$  to compute  $C3$  and  $S2$  ( $0 + 1 + 1 = 10$ )
5. Use  $C3$  to compute  $CO$  and  $S3$  ( $1 + 1 + 1 = 11$ )
 
## Ripple carry delays

- The diagram below shows our four-bit adder completely drawn out.
- This is called a **ripple carry adder**, because the inputs A0, B0 and C1 "ripple" leftwards until C0 and S3 are produced.
- Ripple carry adders are slow!
  - There is a very long path from A0, B0 and C1 to C0 and S3.
  - For an  $n$ -bit ripple carry adder, the longest path has  $2n+1$  gates.
  - The longest path in a 64-bit adder would include 129 gates!



## A faster way to compute carry outs

- Instead of waiting for the carry out from each previous stage, we can minimize the delay by computing it directly with a two-level circuit.
- First we'll define two functions.
  - The "generate" function  $G_i$  produces 1 when there *must* be a carry out from position  $i$  (i.e., when  $A_i$  and  $B_i$  are both 1).


$$G_i = A_i B_i$$

- The "propagate" function  $P_i$  is true when an incoming carry is propagated (i.e, when  $A_i=1$  or  $B_i=1$ , but not both).

$$P_i = A_i \oplus B_i$$

- Then we can rewrite the carry out function.

$$C_{i+1} = G_i + P_i C_i$$

 

$A_i$	$B_i$	$C_i$	$C_{i+1}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- Let's look at the carry out equations for specific bits, using the general equation from the previous page  $C_{i+1} = G_i + P_i C_i$ .

$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 \\ &= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

- These expressions are all sums of products, so we can use them to make a circuit with only a two-level delay.

 


Fig. 4-11 Logic Diagram of Carry Lookahead Generator


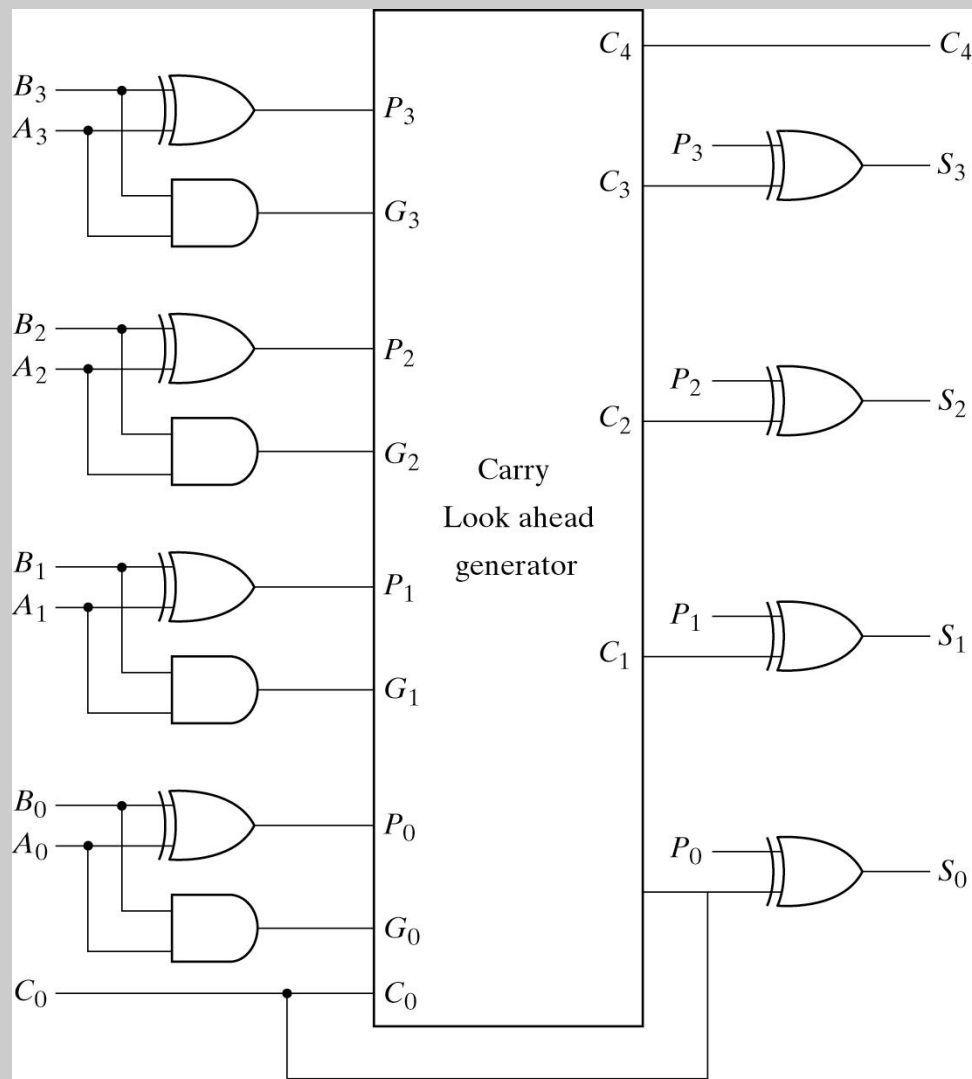



Fig. 4-12 4-Bit Adder with Carry Lookahead

## A faster four-bit adder

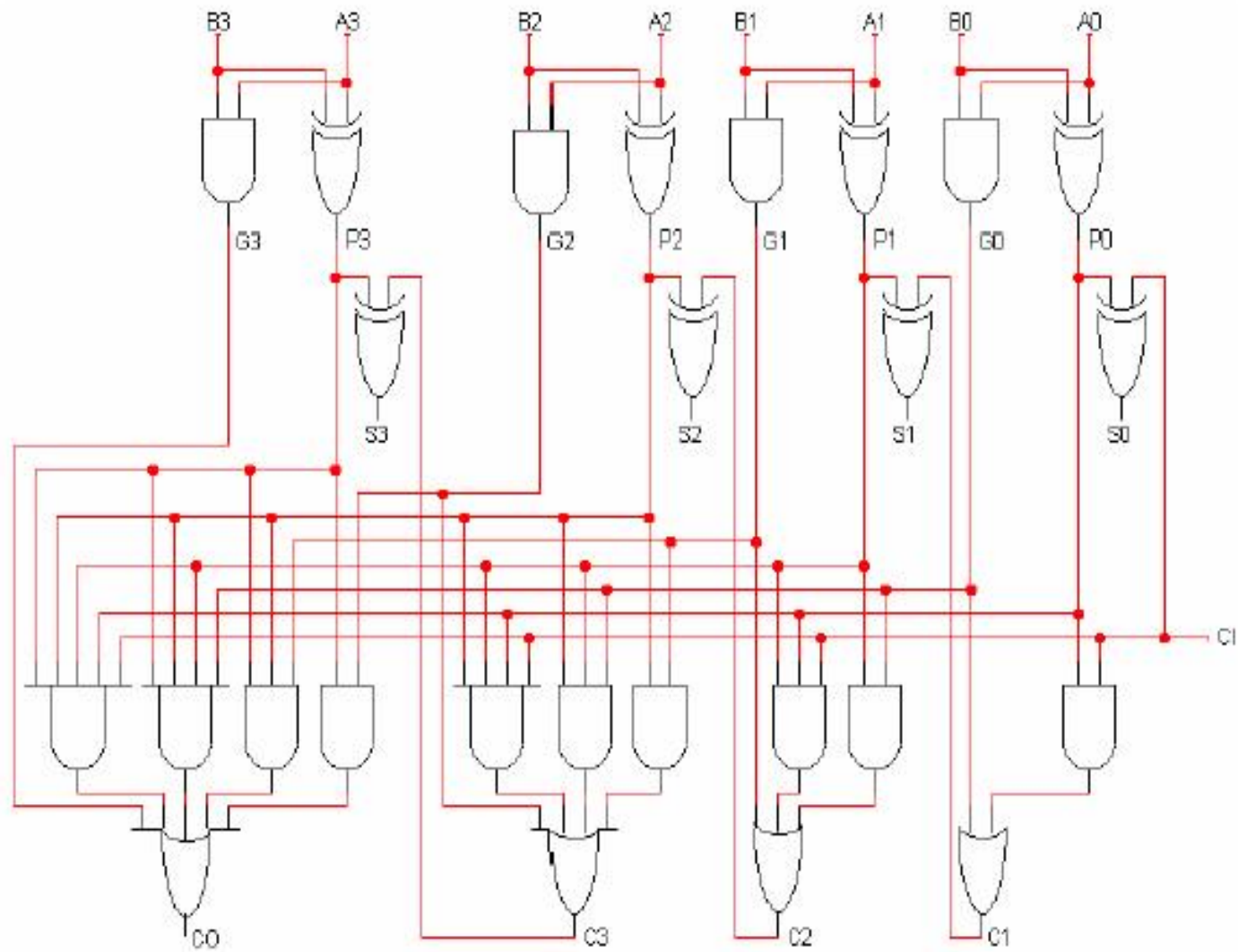




## A four-bit adder

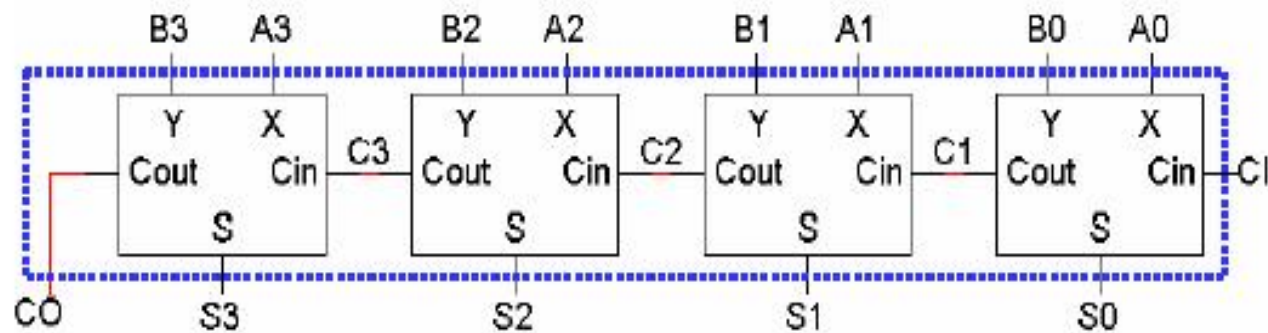

 
- Similarly, we can cascade four full adders to build a four-bit adder.
  - The inputs are two four-bit numbers ( $A_3A_2A_1A_0$  and  $B_3B_2B_1B_0$ ) and a carry in  $Cl$ .
  - The two outputs are a four-bit sum  $S_3S_2S_1S_0$  and the carry out  $CO$ .
- If you designed this adder without taking advantage of the hierarchical structure, you'd end up with a 512-row truth table with five outputs!




 
## An example of 4-bit addition


- Let's put our initial example into this circuit, with  $A=1011$  and  $B=1110$ .




1. Fill in all the inputs, including  $CI=0$
2. The circuit produces  $C1$  and  $S0$  ( $1 + 0 + 0 = 01$ )
3. Use  $C1$  to find  $C2$  and  $S1$  ( $1 + 1 + 0 = 10$ )
4. Use  $C2$  to compute  $C3$  and  $S2$  ( $0 + 1 + 1 = 10$ )
5. Use  $C3$  to compute  $CO$  and  $S3$  ( $1 + 1 + 1 = 11$ )

# Integrated Circuit Parallel Adder ( IC Parallel Adder )

## 4- Bits adder

 

# 8 – Bit IC Parallel Adder

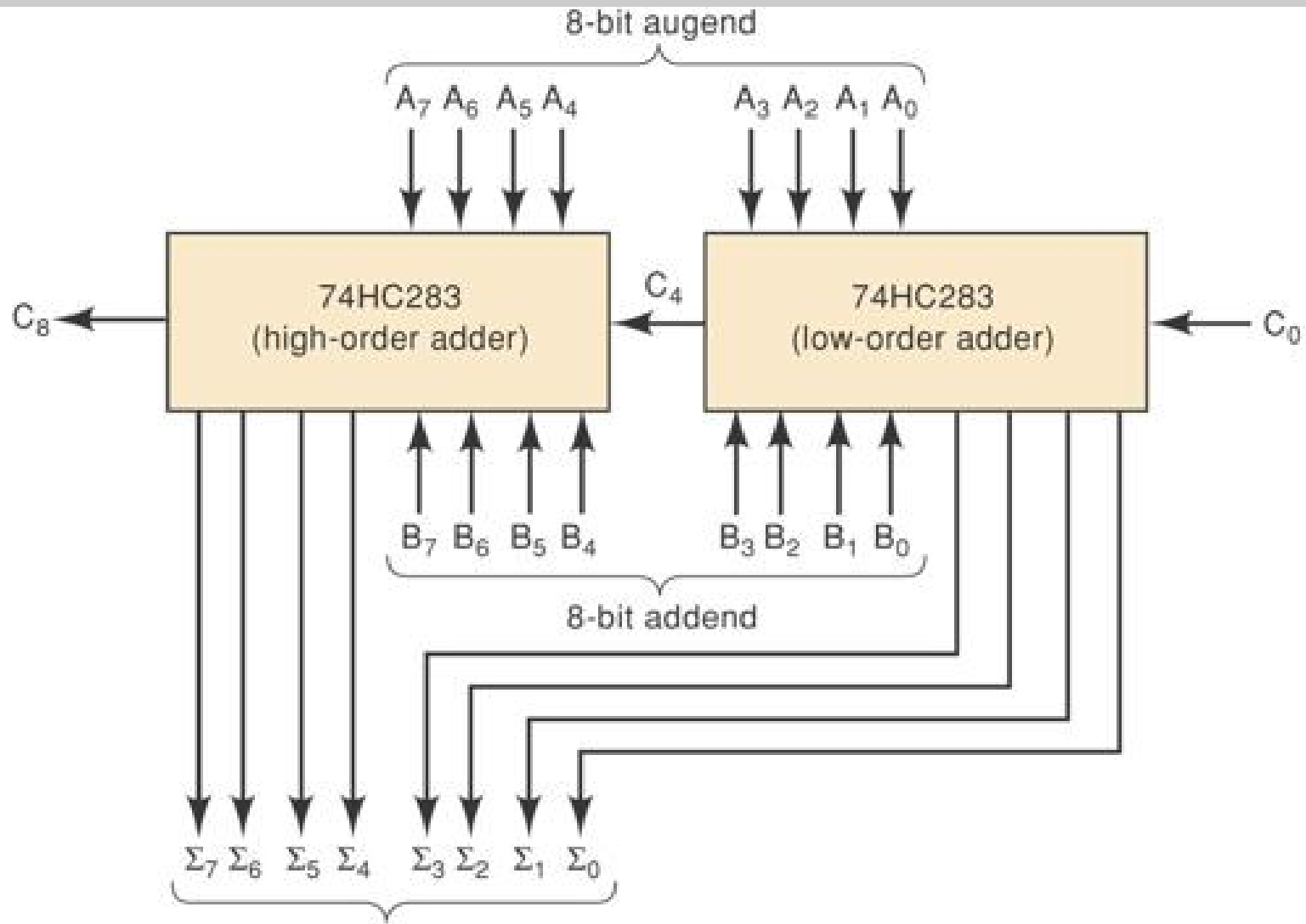

# Binary Adder/Subtractors

- The subtraction  $A-B$  can be performed by taking the 2's complement of  $B$  and adding to  $A$ .
- The 2's complement of  $B$  can be obtained by complementing  $B$  and adding one to the result.

$$\begin{aligned}A-B &= A + 2C(B) \\ &= A + 1C(B) + 1 \\ &= A + B' + 1\end{aligned}$$

# Binary Adder/Subtractors

Representation of numbers

# Representation

- 2's Complement
  - x:  $2^n - x$
- 1's Complement
  - x:  $2^n - x - 1$

# Representation

- 2's Complement

$-x: 2^n - x$

e.g.  $16 - x$

- 1's Complement

$-x: 2^n - x - 1$

e.g.  $16 - x - 1$

Id	2's comp.	1's comp.
0	0	15
-1	15	14
-2	14	13
-3	13	12
-4	12	11
-5	11	10
-6	10	9
-7	9	8
-8	8	

# Representation

Id	-Binary	sign mag	2's comp	1's comp
0	0000	1000	0000	1111
-1	0001	1001	1111	1110
-2	0010	1010	1110	1101
-3	0011	1011	1101	1100
-4	0100	1100	1100	1011
-5	0101	1101	1011	1010
-6	0110	1110	1010	1001
-7	0111	1111	1001	1000
-8			1000	



# Representation

## 1's Complement

For a negative number, we take the positive number and complement every bit.

## 2's Complement

For a negative number, we do 1's complement and plus one.

$$(b_{n-1}, b_{n-2}, \dots, b_0): -b_{n-1}2^{n-1} + \sum_{i < n-1} b_i 2^i$$

# Representation

## 2's Complement

- $x+y$
- $x-y: x+2^n-y=2^n+x-y$
- $-x+y: 2^n-x+y$
- $-x-y: 2^n-x+2^n-y$   
 $= 2^n+2^n-x-y$
- $-(-x)=2^n-(2^n-x)=x$

## 1's Complement

- $x+y$
- $x-y: x+2^n-y-1=2^n-1+x-y$
- $-x+y: 2^n-x-1+y=2^n-1-x+y$
- $-x-y: 2^n-x-1+2^n-y-1$   
 $= 2^n-1+2^n-x-y-1$
- $-(-x)=2^n-(2^n-x-1)-1=x$

# Examples

$$\begin{array}{r}
 2 + 3 = 5 \\
 \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{0} \\
 \phantom{+} 0 \text{ } 0 \text{ } 1 \text{ } 0 \\
 + \phantom{0} 0 \text{ } 0 \text{ } 1 \text{ } 1 \\
 \hline
 0 \text{ } 1 \text{ } 0 \text{ } 1
 \end{array}$$

$$\begin{array}{r}
 2 - 3 = -1 \text{ (2's)} \\
 \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{0} \\
 \phantom{+} 0 \text{ } 0 \text{ } 1 \text{ } 0 \\
 + \phantom{0} 1 \text{ } 1 \text{ } 0 \text{ } 1 \\
 \hline
 1 \text{ } 1 \text{ } 1 \text{ } 1
 \end{array}$$

$$\begin{array}{r}
 2 - 3 = -1 \text{ (1's)} \\
 \phantom{+} 0 \text{ } 0 \text{ } 1 \text{ } 0 \\
 + \phantom{0} 1 \text{ } 1 \text{ } 0 \text{ } 0 \\
 \hline
 1 \text{ } 1 \text{ } 1 \text{ } 0
 \end{array}$$

Check for overflow (2's)

$$\begin{array}{r}
 -2 - 3 = -5 \text{ (2's)} \\
 \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{0} \\
 \phantom{+} 1 \text{ } 1 \text{ } 1 \text{ } 0 \\
 + \phantom{0} 1 \text{ } 1 \text{ } 0 \text{ } 1 \\
 \hline
 1 \text{ } 0 \text{ } 1 \text{ } 1
 \end{array}$$

$$\begin{array}{r}
 -2 - 3 = -5 \text{ (1's)} \\
 \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{0} \\
 \phantom{+} 1 \text{ } 1 \text{ } 0 \text{ } 1 \\
 + \phantom{0} 1 \text{ } 1 \text{ } 0 \text{ } 0 \\
 \hline
 1 \text{ } 0 \text{ } 0 \text{ } 1 \\
 \phantom{+} \phantom{0} \phantom{0} \phantom{0} \textcolor{red}{1} \\
 \hline
 1 \text{ } 0 \text{ } 1 \text{ } 0
 \end{array}$$

$$\begin{array}{r}
 3 + 5 = 8 \\
 \textcolor{red}{0} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \\
 \phantom{+} 0 \text{ } 0 \text{ } 1 \text{ } 1 \\
 + \phantom{0} 0 \text{ } 1 \text{ } 0 \text{ } 1 \\
 \hline
 1 \text{ } 0 \text{ } 0 \text{ } 0 \\
 \text{C}_4\text{C}_3
 \end{array}$$

$$\begin{array}{r}
 -3 + -5 = -8 \\
 \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \\
 \phantom{+} 1 \text{ } 1 \text{ } 0 \text{ } 1 \\
 + \phantom{0} 1 \text{ } 0 \text{ } 1 \text{ } 1 \\
 \hline
 1 \text{ } 0 \text{ } 0 \text{ } 0 \\
 \text{C}_4\text{C}_3
 \end{array}$$

# Addition: 2's Complement Overflow


In 2's complement:

$$\text{overflow} = c_n \text{ xor } c_{n-1}$$

Exercise:


1. Demonstrate the overflow with more examples.
2. Prove the condition.
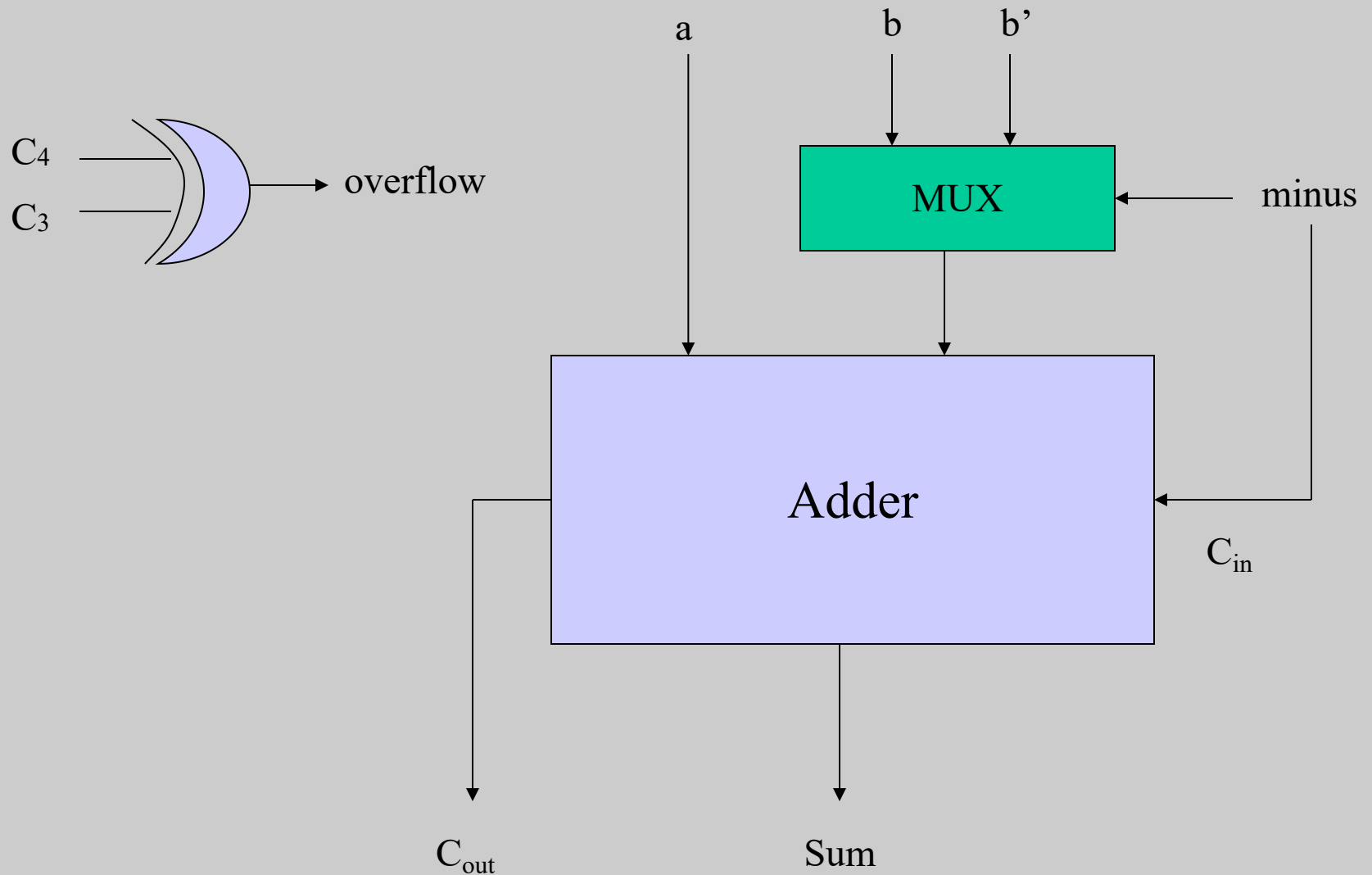
# Addition and Subtraction using 2's Complement



# 1-Bit Adders

## Half Adder

 


A	B	$C_{out}$	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

## Full Adder

 


$C_{in}$	A	B	$C_{out}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

# 4-bit Binary Adder/Subtractor

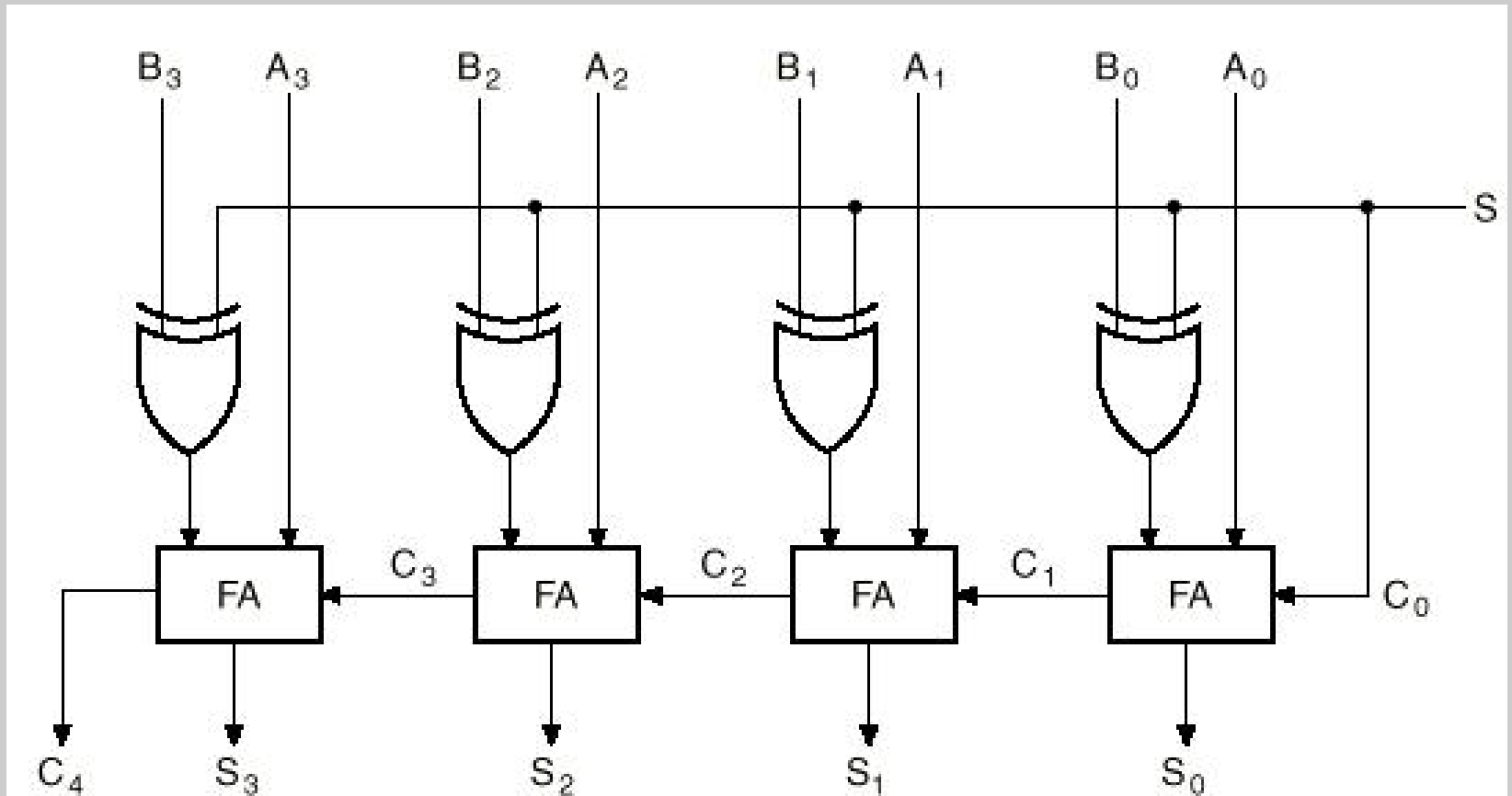


-XOR gates act as programmable inverters

## 4-bit Binary Adder/Subtractor (cont.)

- When  $S=0$ , the circuit performs  $A + B$ . The carry in is 0, and the XOR gates simply pass  $B$  untouched.
- When  $S=1$ , the carry into the least significant bit (LSB) is 1, and  $B$  is complemented (1's complement) prior to the addition; hence, the circuit adds to  $A$  the 1's complement of  $B$  plus 1 (from the carry into the LSB).




## 4-bit Binary Adder/Subtractor (cont.)

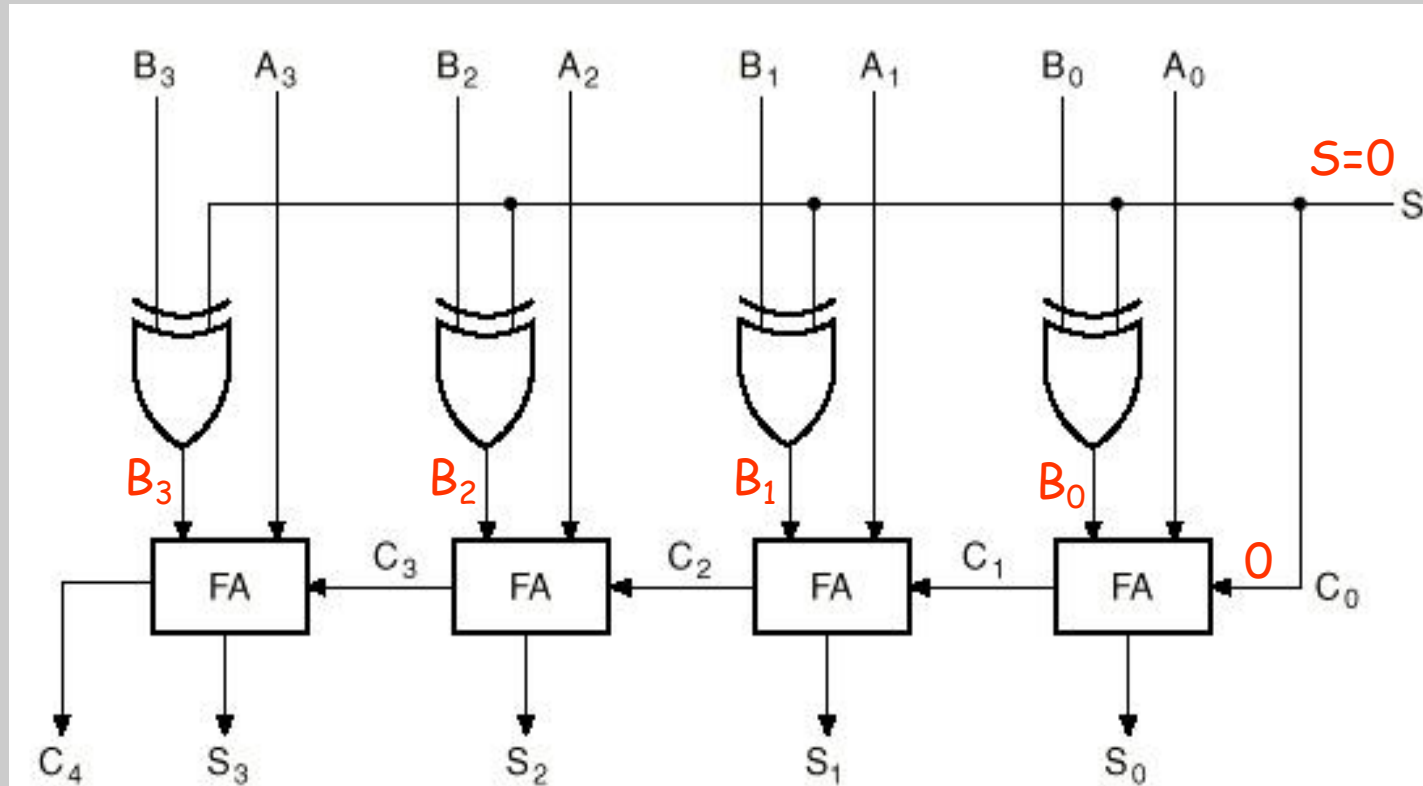

S=0 selects addition

# 4-bit Binary Adder/Subtractor (cont.)

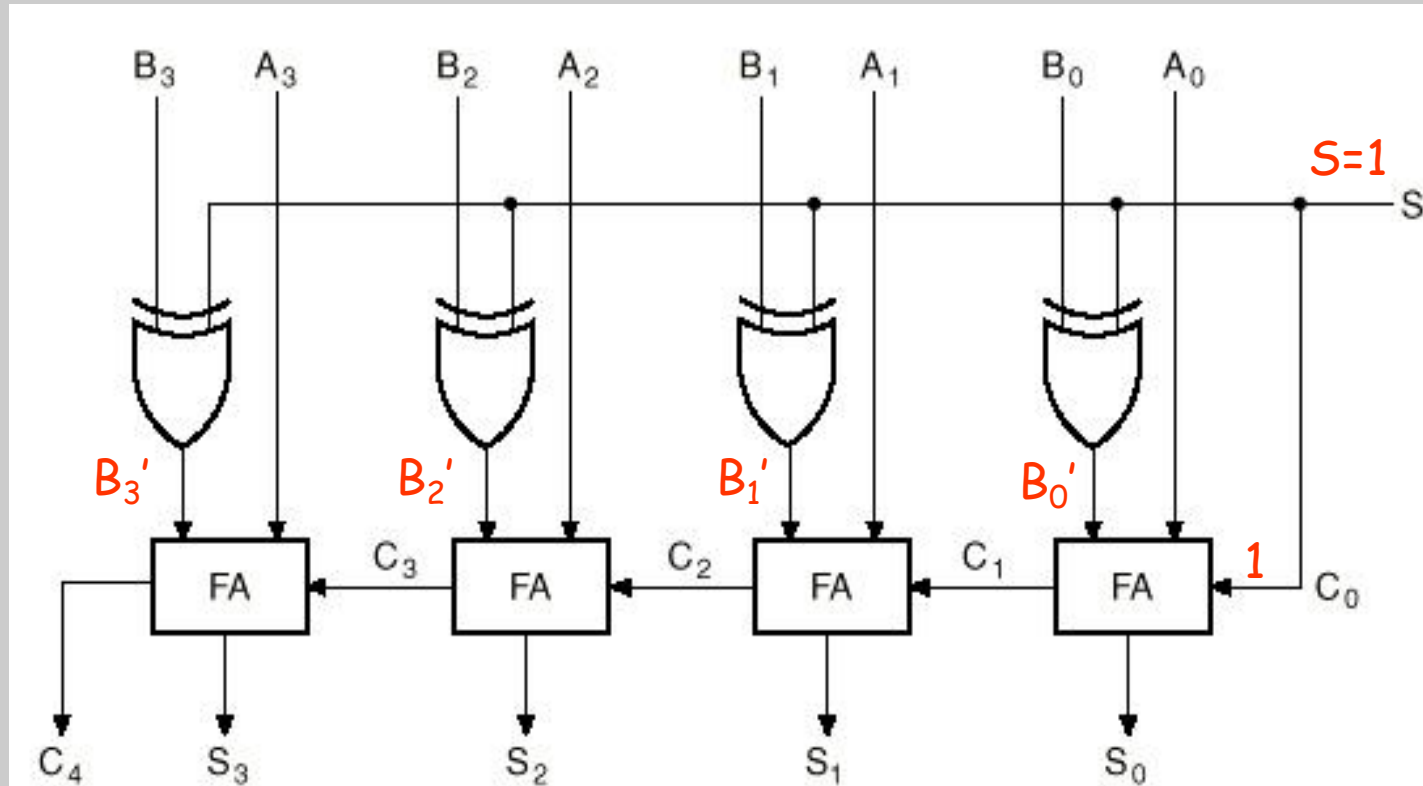

$S=1$  selects subtraction


## Parallel Binary adder

Two Numbers X & Y

Each number is represented using 6 bits.


$$[X] = X_0 X_1 X_2 X_3 X_4 X_5$$

$$[Y] = Y_0 Y_1 Y_2 Y_3 Y_4 Y_5$$

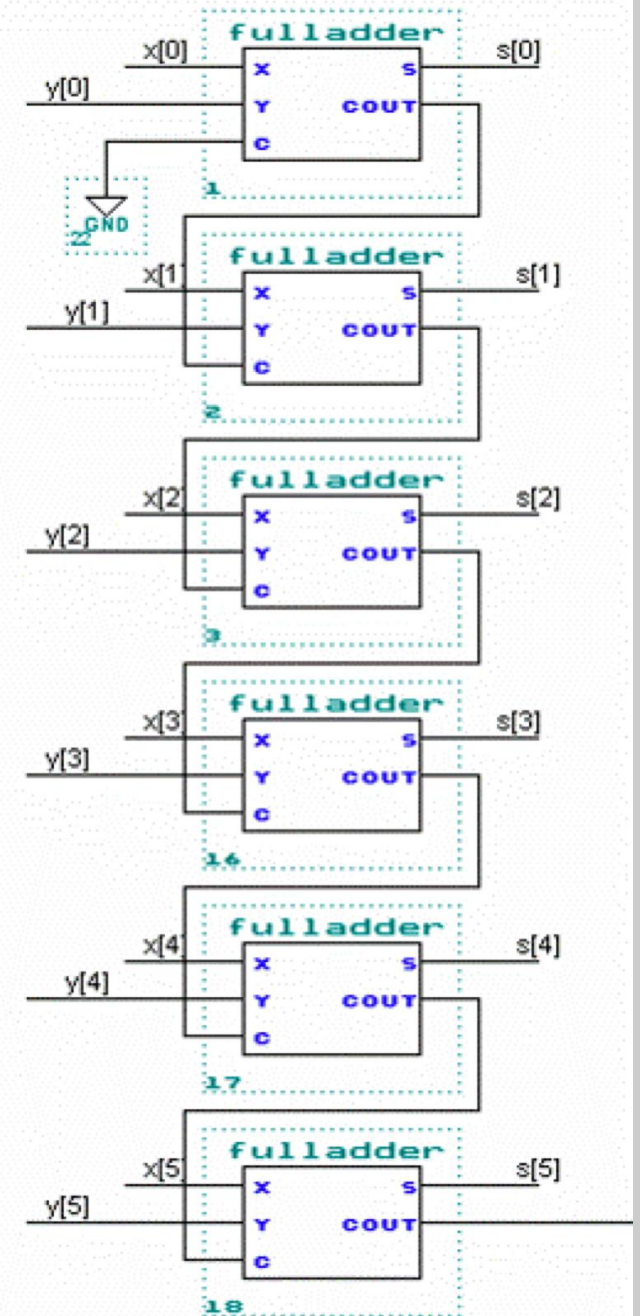
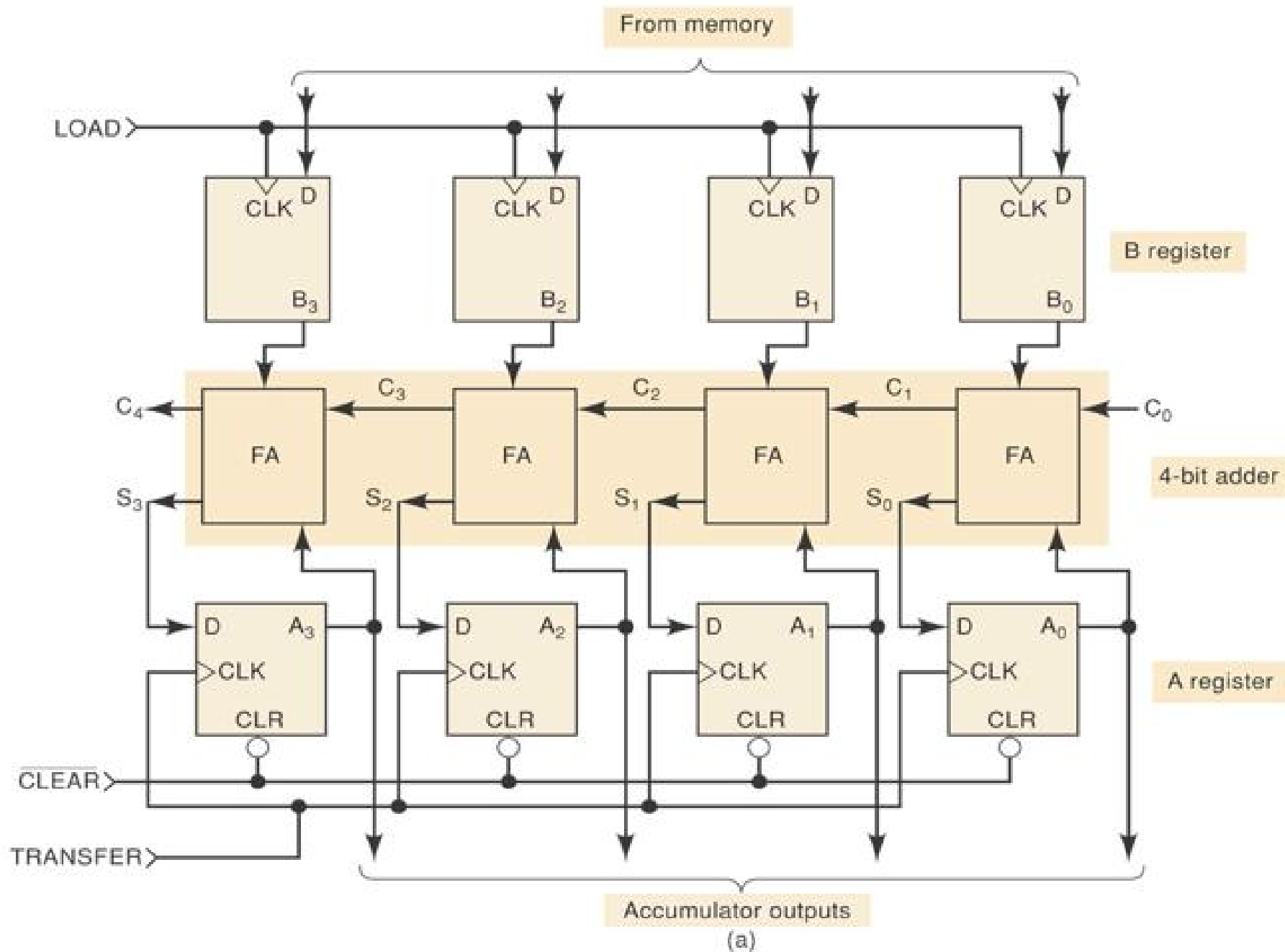
# **Complete Parallel Adder With Registers**

- D Flip-flops are used to save a single bit
- A number of D flip-flops are connected in a way to form the binary number, where each bit of that number is saved in a single D flip-flop.




# Example: Sequence of operations in Adding 1001 and 0101


- 1)  $[A] = 0000$ . A CLEAR pulse is applied to CLR of each FF on register A at  $t_1$ .
- 2)  $[M] \rightarrow [B]$ . The first binary number 1001 is transferred from memory to B register on the PGT of the LOAD pulse at  $t_2$ .
- 3)  $[S] \rightarrow [A]$ . With  $[B] = 1001$  and  $[A] = 0000$ , the full adders produce a sum of 1001 which is transferred to A register on the PGT of the TRANSFER pulse at  $t_3$ . This makes  $[A] = 1001$ .
- 4)  $[M] \rightarrow [B]$ . The second binary number 0101 is transferred from memory to B register on the PGT of the second LOAD pulse at  $t_4$ . This makes  $[B] = 0101$ .
- 5)  $[S] \rightarrow [A]$ . With  $[B] = 0101$  and  $[A] = 1001$ , the full adders produce a sum of 1110 which is transferred to A register on the PGT of the second TRANSFER pulse at  $t_5$ . This makes  $[A] = 1110$ .

# Integrated Circuit Parallel Adder ( IC Parallel Adder )

## 4- Bits adder

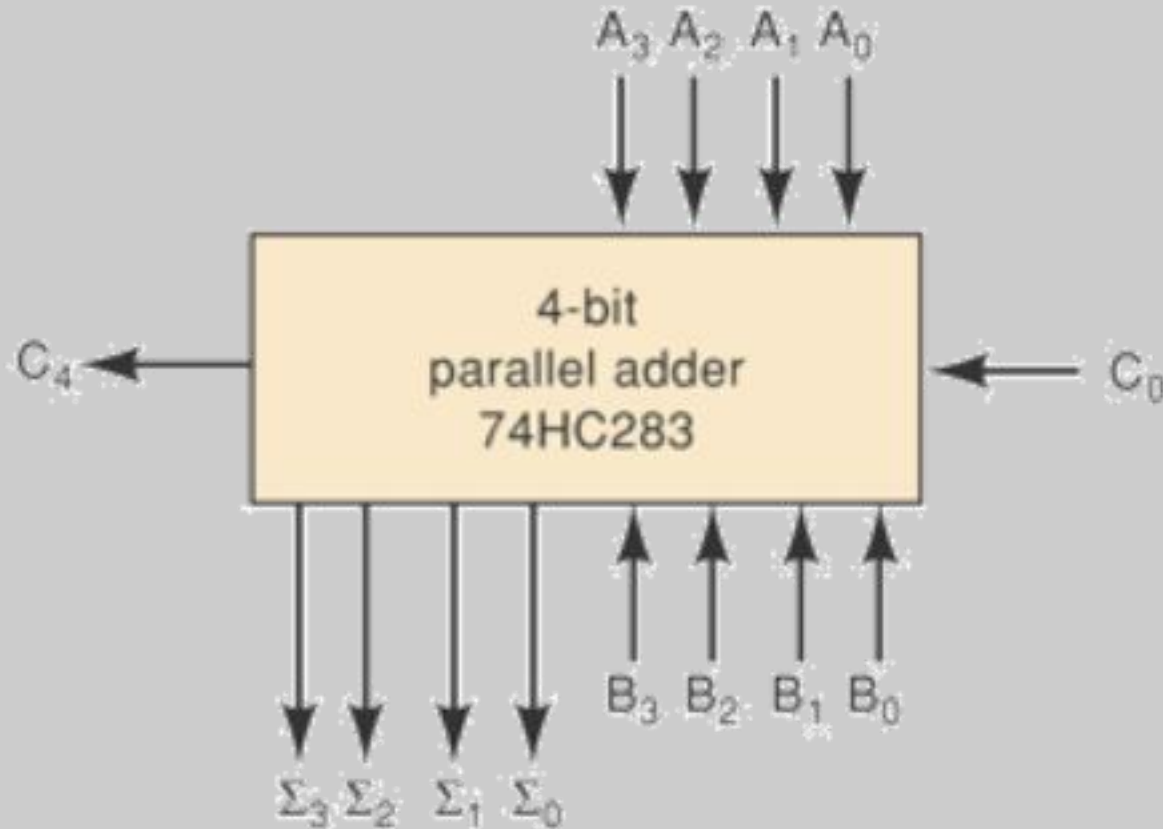

# 8 – Bit IC Parallel Adder

 




# Conversion and Coding

$(12)_{10}$

# Conversion and Coding


$(12)_{10}$

 

Conversion

1100

# Conversion and Coding

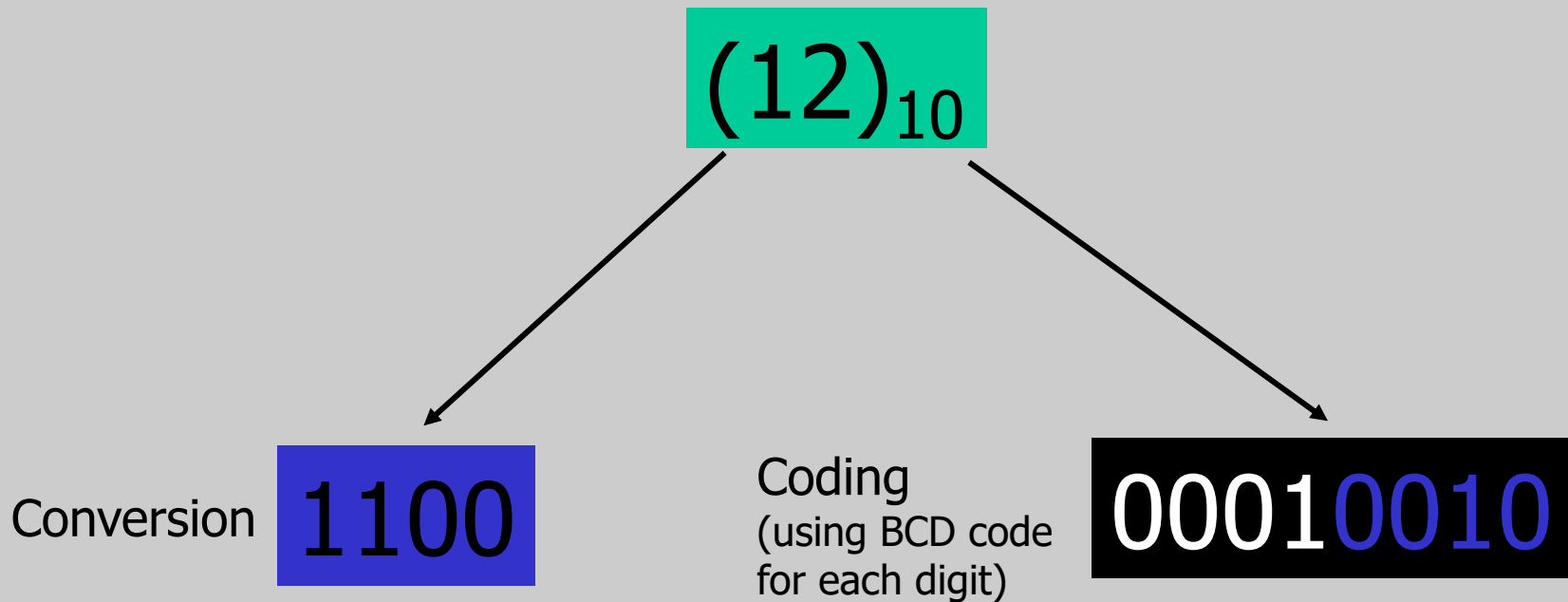

# BCD Adder

Design a circuit that calculates the Arithmetic addition of two decimal digits.

$$\begin{array}{r} 9 \\ + 3 \\ \hline 2 \end{array}$$

1  
carry

# BCD Adder

Design a circuit that calculates the Arithmetic addition of two decimal digits.

$\begin{array}{r} 6 \\ + 3 \\ \hline 9 \end{array}$	$\begin{array}{r} 0110 \\ + 0011 \\ \hline 1001 \end{array}$	<div style="display: inline-block; text-align: center;"> <div style="color: teal;">→</div>BCD         </div>	$\begin{array}{r} 9 \\ + 3 \\ \hline 12 \end{array}$	$\begin{array}{r} 1001 \text{ BCD} \\ + 0011 \text{ BCD} \\ \hline 1100 \end{array}$	<div style="display: inline-block; text-align: center;"> <div style="color: red;">1</div> </div>	$\begin{array}{r} 1100 \text{ not BCD} \\ + 0110 \\ \hline 0001 \end{array}$
---	--	--	--	--	--	--

- If sum is up to 9: Use the regular Adder.
- If the sum > 9: Use the regular adder and add 6 to the result


Correction Adder

$$\begin{array}{r} 0001 \\ + 0110 \\ \hline 0011 \end{array}$$

1
2

# BCD Adder

- Maximum sum is  $9+9 + 1 = 19$

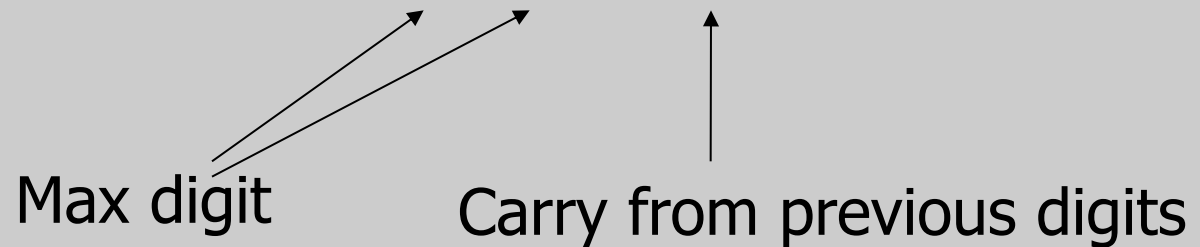

Max digit                      Carry from previous digits

# BCD adder (sum up to 9)

Number	C	S8	S4	S2	S1
0	0	0	0	0	0
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	0	1	1
4	0	0	1	0	0
5	0	0	1	0	1
6	0	0	1	1	0
7	0	0	1	1	1
8	0	1	0	0	0
9	0	1	0	0	1

# BCD adder (sum up to 9)

Number	C	S8	S4	S2	S1
0	0	0	0	0	0
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	0	1	1
4	0	0	1	0	0
5	0	0	1	0	1
6	0	0	1	1	0
7	0	0	1	1	1
8	0	1	0	0	0
9	0	1	0	0	1

The sum is the same with BCD



# BCD adder (sum is 10 to 19)

Number	C	S8	S4	S2	S1
10	1	0	0	0	0
11	1	0	0	0	1
12	1	0	0	1	0
13	1	0	0	1	1
14	1	0	1	0	0
15	1	0	1	0	1
16	1	0	1	1	0
17	1	0	1	1	1
18	1	1	0	0	0
19	1	1	0	0	1

# BCD adder (sum is 10 to 19)

## BCD adder sum

Number	C	S8	S4	S2	S1
10	1	0	0	0	0
11	1	0	0	0	1
12	1	0	0	1	0
13	1	0	0	1	1
14	1	0	1	0	0
15	1	0	1	0	1
16	1	0	1	1	0
17	1	0	1	1	1
18	1	1	0	0	0
19	1	1	0	0	1

## Binary sum

K	Z8	Z4	Z2	Z1
0	1	0	1	0
0	1	0	1	1
0	1	1	0	0
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1


# BCD adder (sum is 10 to 19)

BCD adder sum

Number	C	S8	S4	S2	S1
10	1	0	0	0	0
11	1	0	0	0	1
12	1	0	0	1	0
13	1	0	0	1	1
14	1	0	1	0	0
15	1	0	1	0	1
16	1	0	1	1	0
17	1	0	1	1	1
18	1	1	0	0	0
19	1	1	0	0	1

Binary sum

K	Z8	Z4	Z2	Z1
0	1	0	1	0
0	1	0	1	1
0	1	1	0	0
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1

 

# BCD adder (sum is 10 to 19)

BCD adder sum

Number	C	S8	S4	S2	S1
10	1	0	0	0	0
11	1	0	0	0	1
12	1	0	0	1	0
13	1	0	0	1	1
14	1	0	1	0	0
15	1	0	1	0	1
16	1	0	1	1	0
17	1	0	1	1	1
18	1	1	0	0	0
19	1	1	0	0	1

+6

Binary sum

K	Z8	Z4	Z2	Z1
0	1	0	1	0
0	1	0	1	1
0	1	1	0	0
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1

# Algorithm for BCD Adder

- If sum is up to 9
  - Use the regular Adder.
- If the sum  $> 9$ 
  - Use the regular adder and add 6 to the result

# When is the result $> 9$

Binary sum

Number	K	Z8	Z4	Z2	Z1
10	0	1	0	1	0
11	0	1	0	1	1
12	0	1	1	0	0
13	0	1	1	0	1
14	0	1	1	1	0
15	0	1	1	1	1
16	1	0	0	0	0
17	1	0	0	0	1
18	1	0	0	1	0
19	1	0	0	1	1

$C = K +$

# When is the result $> 9$

Binary sum

Number	K	Z8	Z4	Z2	Z1
10	0	1	0	1	0
11	0	1	0	1	1
12	0	1	1	0	0
13	0	1	1	0	1
14	0	1	1	1	0
15	0	1	1	1	1
16	1	0	0	0	0
17	1	0	0	0	1
18	1	0	0	1	0
19	1	0	0	1	1

$$C = K + Z8 * Z4$$

# When is the result $> 9$


Binary sum

Number	K	Z8	Z4	Z2	Z1
10	0	1	0	1	0
11	0	1	0	1	1
12	0	1	1	0	0
13	0	1	1	0	1
14	0	1	1	1	0
15	0	1	1	1	1
16	1	0	0	0	0
17	1	0	0	0	1
18	1	0	0	1	0
19	1	0	0	1	1

$$C = K + Z8 * Z4 - Z8 * Z2$$



# BCD Adder

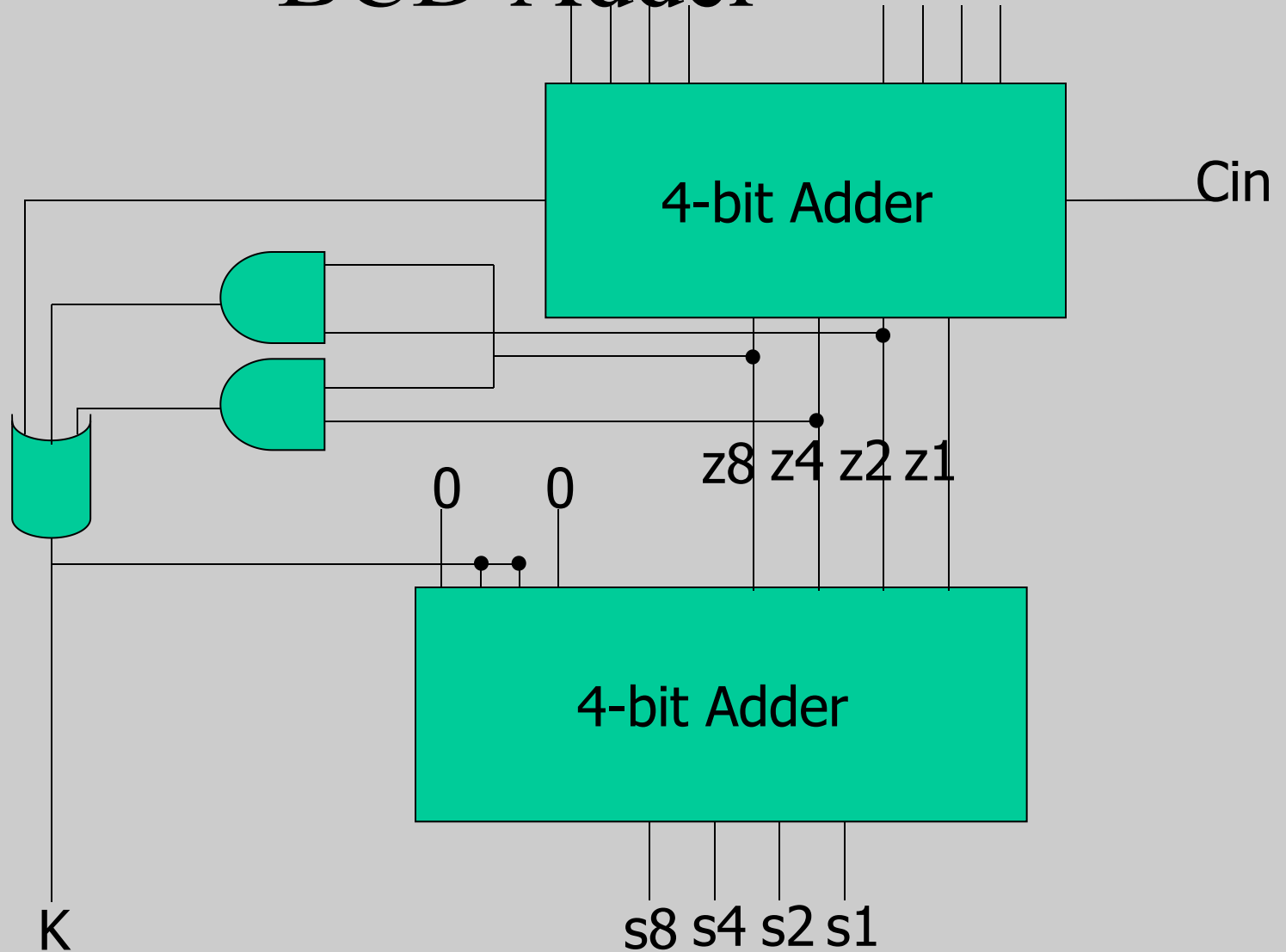

# BCD Adder

# BCD Adder

- When the sum of two digits is less than or equal to 9 then the ordinary 4-bit adder can be used
- But if the sum of two digits is greater than 9 then a correction must be added “I.e adding 0110”
- We need to design a circuit that is capable of doing the correct addition

# BCD Adder

- The cases where the sum of two 4-bit numbers is greater than 9 are in the following table:

S <sub>4</sub>	S <sub>3</sub>	S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	
0	1	0	1	0	10
0	1	0	1	1	11
0	1	1	0	0	12
0	1	1	0	1	13
0	1	1	1	0	14
0	1	1	1	1	15
1	0	0	0	0	16
1	0	0	0	1	17
1	0	0	1	0	18


# BCD Adder

- Whenever  $S_4=1$  (sums greater than 15)
- Whenever  $S_3=1$  and either  $S_2$  or  $S_1$  or both are 1 (sums 10 to 15)
- The previous table can be expressed as:


$$X = S_4 + S_3 ( S_2 + S_1 )$$

So, whenever  $X = 1$  we should add a correction of 0110 to the sum.

Inputs: [A]=0101, [B]= 0011,  $C_0=0$

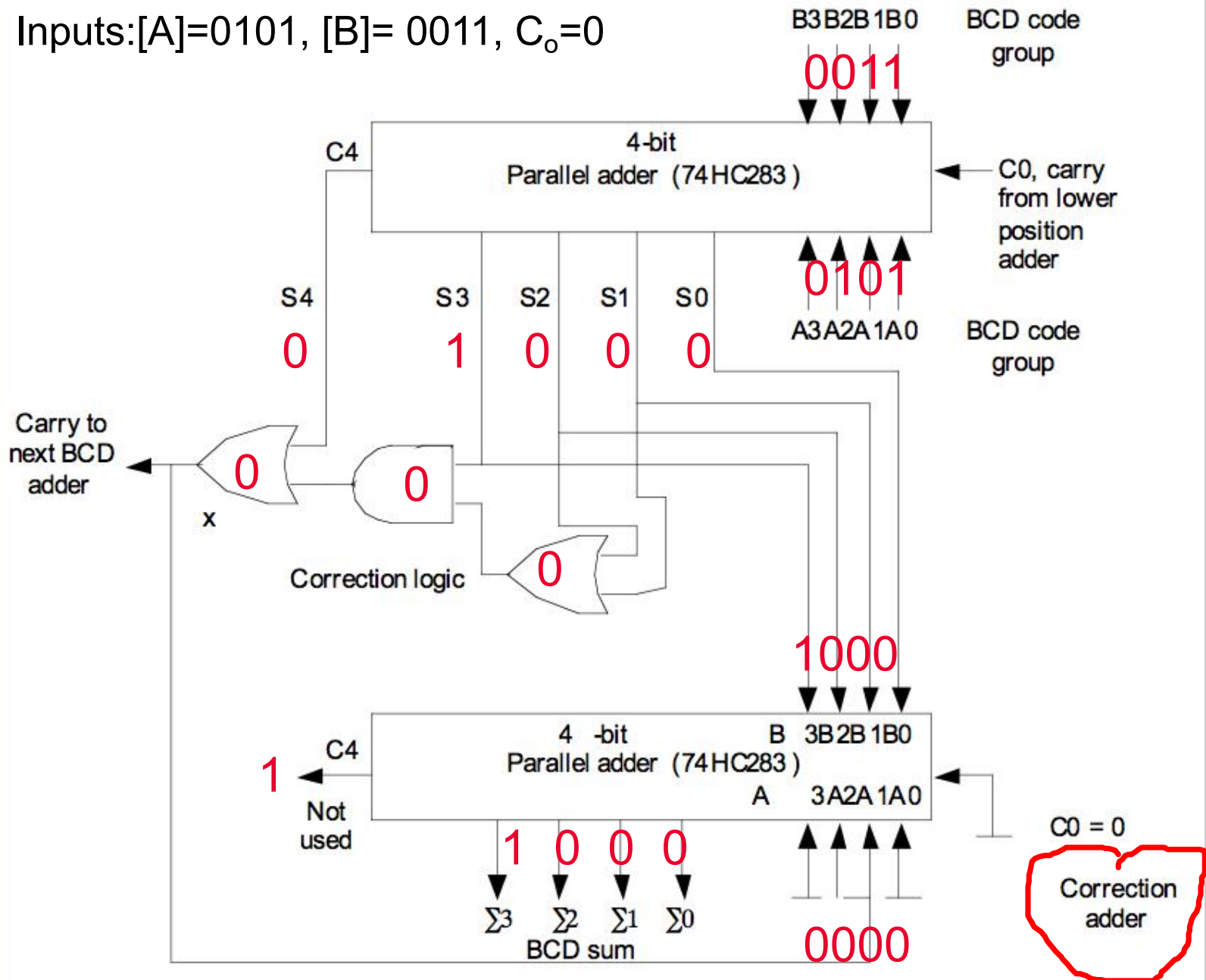


Inputs: [A]=0111, [B]= 0110,  $C_0=0$

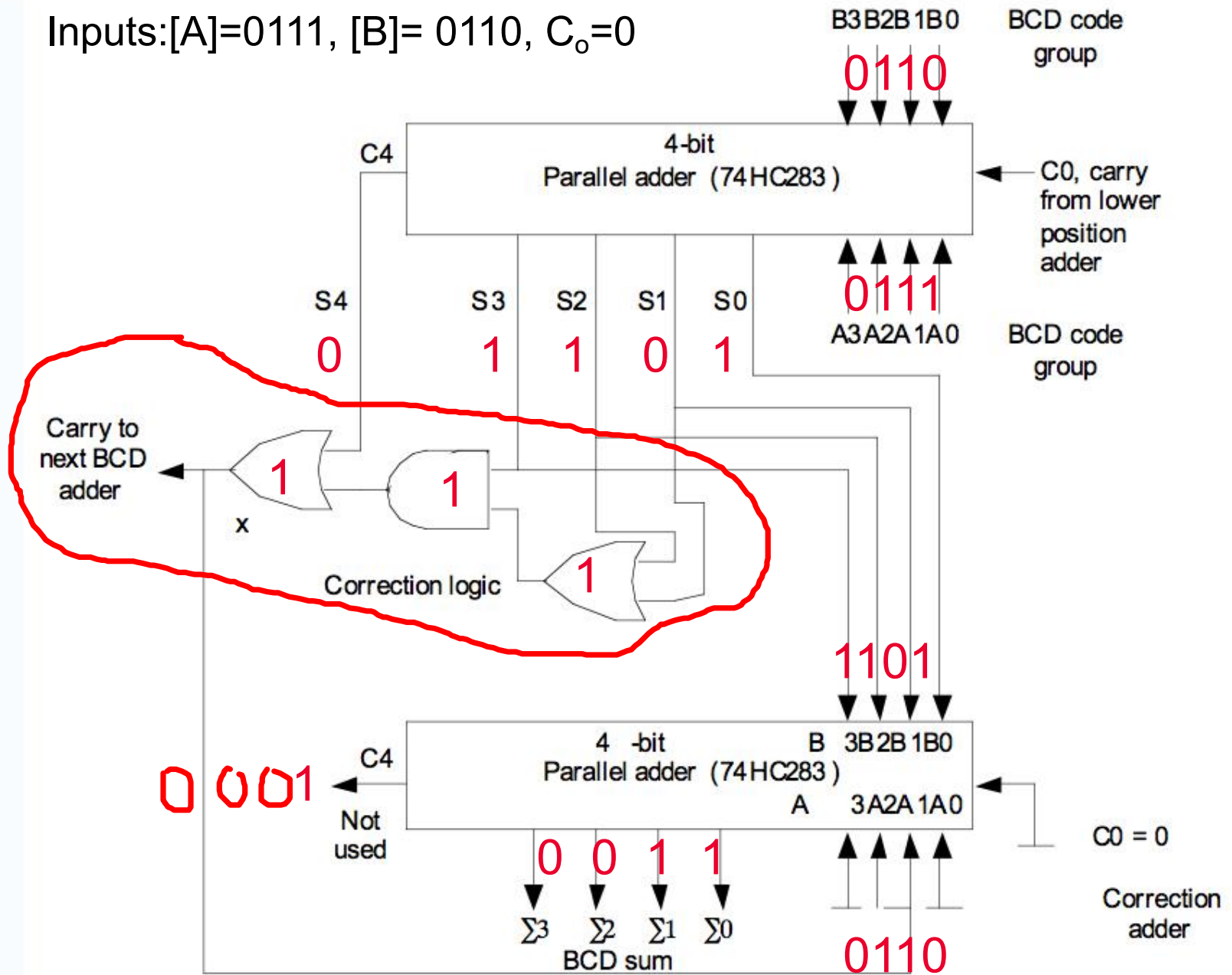

 
# Cascading BCD Adders

- The previous circuit is used for adding two decimal digits only. That is, “ $7 + 6 = 13$ ”.
- For adding numbers with several digits, a separate BCD adder for each digit position must be used.
- For example:





# Cascading BCD Adders

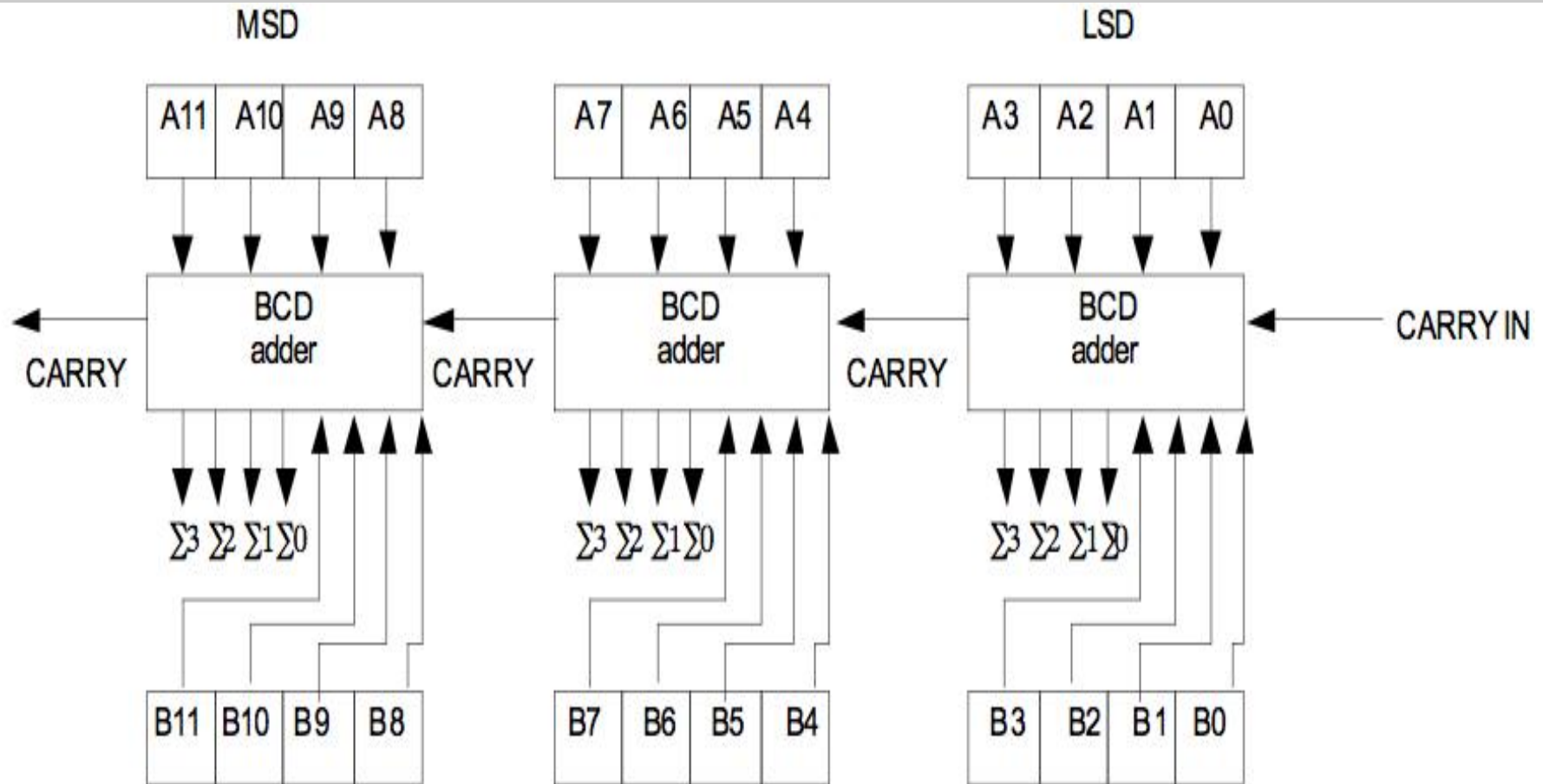

# Example

- Determine the inputs and the outputs when the above circuit is used to add 538 to 247.

Assume a CARRY IN = 0

- Solution:

– Represent the decimal numbers in BCD

$$247 = 0010 \ 0100 \ 0111$$


$$538 = 0101 \ 0011 \ 1000$$

Put these numbers in registers [A] and [B]

$$[A] = 0010 \ 0100 \ 0111$$

$$[B] = 0101 \ 0011 \ 1000$$

# Example

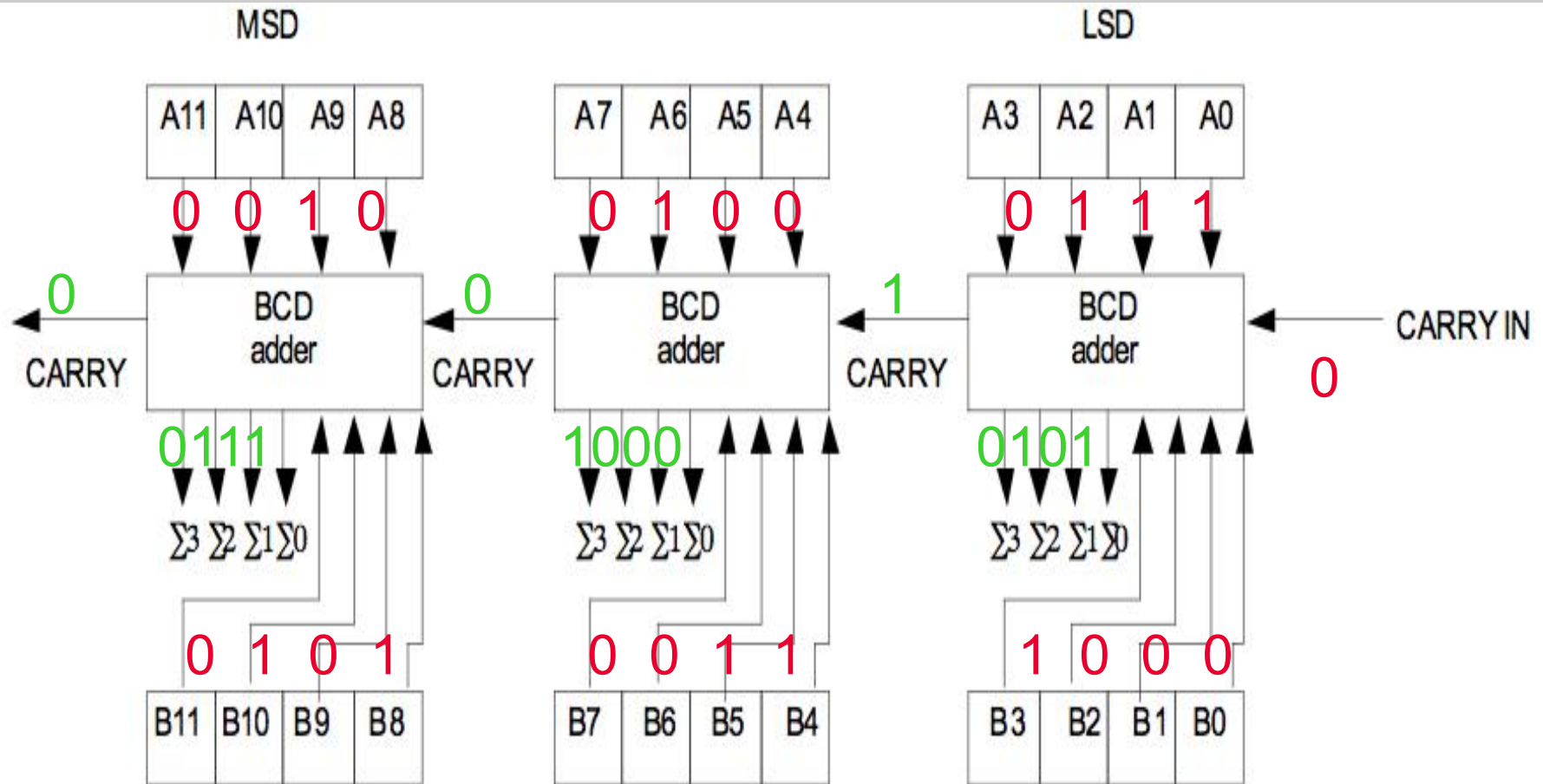

# Two's compliment

- But how do you represent a minus sign electronically in a computer?
- How can you represent it such that arithmetic operations are manageable?
- There are two types of compliments for each number base system.
  - Have the  $r$ 's complement
  - Have the  $(r-1)$ 's complement
- For base 2 have 2's complement and 1's complement

# 1's Complement

- 1's complement of N is defined as  $(2^n - 1) - N$ .
  - If  $n=4$  have  $(2^n - 1)$  being  $1\ 0000 - 1 = 1111$
- So for  $n=4$  would subtract any 4-bit binary number from  $1111$ .
- This is just inverting each bit.
- Example: 1's complement of  $1011001$
- is  $0100110$

## 1's Complement

**For a negative number, we take the positive number and complement every bit.**

# 2's complement

- The 2's complement is defined as  $2^n - N$
- Can be done by subtraction of  $N$  from  $2^n$  or adding 1 to the 1's complement of a number.
- For  $6 = 0110$ 
  - The 1's complement is 1001
  - The 2's complement is 1010 ( $1001 + 1 = 1010$ )

## 1's Complement

For a negative number, we take the positive number and complement every bit.

## 2's Complement

For a negative number, we do 1's complement and plus one.

# Operation with 2's complement

- Add 4 and -6
- Will use the 2's complement of -6 or 1010

$$\begin{array}{r} + \quad 4 \quad + \quad 0100 \\ + \quad \text{-6} \quad + \quad \underline{1010} \\ \hline -2 \quad 1110 \end{array}$$

- And taking the 2's complement of 1110 get  
 $0001 + 1 = 0010$

# A 2's complement table for 4 bits


- Listing the values represented.

7	0111
6	0110
5	0101
4	0100
3	0011
2	0010
1	0001
0	0000
-1	1111
-2	1110
-3	1101
-4	1100
-5	1011
-6	1010
-7	1001


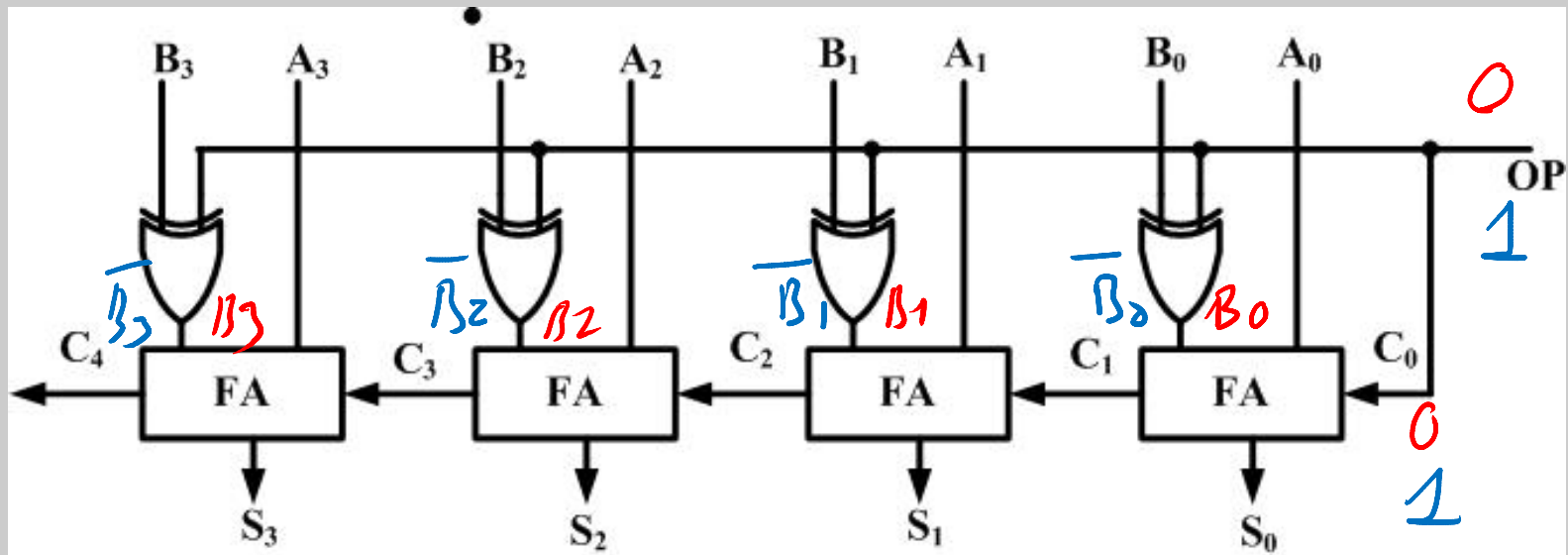
# A circuit that does +/-

- A general adder subtractor
- $OP=0$  for addition/  $=1$  for subtraction



# Another number format

- Signed magnitude – use the MSB to indicate the sign. The remaining bits indicate the magnitude.

No	2s c	sgnd
7	0111	0111
6	0110	0110
5	0101	0101
4	0100	0100
3	0011	0011
2	0010	0010
1	0001	0001
0	0000	0000
-0	nrep	1000
-1	1111	1001
-2	1110	1010
-3	1101	1011
-4	1100	1100
-5	1011	1101
-6	1010	1110
-7	1001	1111

# Overflow

- When adding 2  $n$ -bit numbers it is possible to get a  $n+1$  bit result if there is a carry out.
- On paper it is easy just add another bit.
- In 2's complement add a msb 0 for a positive or a msb 1 for a negative.
- In a computer the number of bits that can be used is fixed.

# Overflow indication.

- In 8-bit 2's complement notation the range that can be represented is -127 to +127.
- Then the operation to add +70 to +80 is

- Carries	0	1	
- +70	0	100	0110
- +80	0	101	0000
			<hr/>
- +150	1	001	0110

- Also look at the addition of -70 and -80


# The other addition

- The addition of -70 and -80

- Carries    1   0
- -70            1  011  1010
- -80            1  011  0000
- -150           0  110  1010

- The rule – if the carry into the msb position differs from the carry out from the msb position then an overflow has occurred

- The circuit

 

- .